

Roll No. ....

3222

B. Tech. 5th Semester (ECE) (Elective-I)  
Examination – March, 2021

LINEAR APPLICATIONS

Paper : PEC-ECE- 313-G

Time : Three hours ]

[ Maximum Marks : 75

*Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.*

*Note : Attempt five questions in all, selecting one question from each Unit. Question No. 1 is compulsory. All questions carry equal marks.*

1. Answer the following in brief : 2.5 × 6 = 15
- (a) What is level translator ?
  - (b) Give ideal characteristics of Op-Amp.
  - (c) What is peaking Op-Amp ? equivalent circuit.
  - (d) Explain summing and scaling Op-Amp. equivalent circuit.
  - (e) Explain high frequency Op-Amp. equivalent circuit.
  - (f) Explain basic differentiator.

3222- 400 -(P-3)(Q-9)(21)

P. T. O.

## UNIT – I

2. Explain working of differential amplifier. Derive equation for DC analysis, AC analysis for single input balanced output differential amplifier. 15
3. (a) Explain the concept of current mirror. 5
- (b) Explain practical characteristics of Op-Amp. 10

## UNIT – II

4. Explain voltage shunt feedback amplifier. Derive equation for closed loop voltage gain, input resistance and output resistance. 15
5. (a) Write note on features of compensating networks. 5
- (b) What is slew rate ? What are its causes ? Derive slew rate equation. 10

## UNIT – III

6. (a) Explain instrumentation amplifier. 10
- (b) Write note on differential input and output amplifier. 5

7. (a) Explain frequency response of basic and practical integrator. 10
- (b) Explain voltage to current converter. 5

#### UNIT – IV

8. Explain pin diagram and internal structure working of 555 timer. 15
9. (a) Explain astable operation of 555 timer. 10
- (b) Explain block diagram of PLL. 5
-

Roll No. ....

**3222**

**B. Tech. (ECE)-(Elective-I) 5th Semester  
Examination – February, 2022**

**LINEAR APPLICATIONS**

**Paper : PEC-ECE-313-G**

*Time : Three Hours ]*

*[ Maximum Marks : 75*

*Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.*

*Note : Question No. 1 is compulsory. Attempt any one question each from Unit-I to Unit-IV.*

1. (a) What are current mirrors ?
- (b) What is a compensating network ?
- (c) Explain voltage to current converter.
- (d) What is instrumentation amplifier ? Give circuit diagram.

3222-650 -(P-3)(Q-9)(22)

P. T. O.

(e) What are the causes of slew rate ?

(f) What is input offset voltage and CMRR ?

$$2.5 \times 6 = 15$$

### UNIT – I

2. Explain working of differential amplifier. Derive equation for DC analysis and AC analysis for dual input, balanced output differential amplifier. 15
3. (a) Explain the concept of level translator. 5
- (b) Give characteristics of ideal Op-Amplifier. 5
- (c) Explain block diagram of Op-Amp. 5

### UNIT – II

4. Explain voltage series feedback amplifier. Derive equation for closed loop voltage gain, input resistance and output resistance. 15
5. Explain high frequency Op-Amp equivalent circuit. What are the sources of capacitive effects ? Derive equation for voltage gain as a function of frequency. 15

### UNIT – III

6. (a) Explain frequency response of basic and practical differentiator. 10
- (b) Write note on peaking and summing amplifier. 5
7. What are active filters ? Derive equation of voltage gain for first order low pass butterworth filter. Write filter design steps. 15

### UNIT – IV

8. Explain pin diagram and internal structure working of 555 timer. 15
9. (a) Explain monostable operation of 555 timer. 10
- (b) Explain operating principle of PLL. 5
-