

Roll No.

3091

**B. Tech. 4th Semester (ECE)
Examination – May, 2023**

ANALOG CIRCUITS

Paper : PCC-ECE-206-G

Time : Three hours]

[Maximum Marks : 75

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Attempt five questions in all, selecting one question from each Section. Question No. 1 is compulsory. All questions carry equal marks.

1. (a) What are various advantages of negative feedback? 4
- (b) Discuss Barkhausen criterion. 4
- (c) What is oxidation process during IC fabrication? 3
- (d) What do you mean by Offset Null in 741 IC. 4

SECTION - I

2. Explain Hybrid Pi model and derive its common emitter short circuit gain. 15
3. Discuss concept of feedback and give general characteristics of -ve feedback. 15

SECTION - II

4. Explain the following : 15
- (a) Wien Bridge Oscillator
 - (b) Colpitts Oscillator.
5. Explain Push Pull amplifiers and Distortion in Push Pull amplifier. 15

SECTION - III

6. Explain series and shunt voltage regulators. 15
7. Discuss various steps used for the process of Integrated circuit fabrication. 15

SECTION – IV

- 8. Explain Block diagram and Pin diagram of OP-Amp and give characteristics of an ideal OP-Amp. 15

 - 9. Explain Input Bias current and Input Offset current of OP-Amp. 15
-

Roll No.

3091

**B. Tech. 4th Semester (ECE)
Examination – July, 2021**

ANALOG CIRCUITS

Paper : PCC-ECE-206-G

Time : Three Hours]

[Maximum Marks : 75

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Attempt five questions in all, selecting one question from each Section. Question No. 1 is compulsory. All questions carry equal marks.

1. (a) Write down the diffusion and ion implantation process. 5
- (b) What is feedback ? Why negative feedback is used in the amplifier ? 3
- (c) What is Barkhausen criteria and its conditions for sustained oscillations ? 3

(d) Define the following terms :

4

- (i) Slew rate
- (ii) Line regulation
- (iii) Minimum load resistance
- (iv) Input bias current

SECTION - I

- 2. Write in detail about the Darlington pair amplifier and derive its main characteristics values. 15
- 3. Why voltage series feedback topology is preferred in practical circuits and prove it mathematically? 15

SECTION - II

- 4. Explain in detail about the phase shift oscillator and derive the conditions for sustained oscillations in it? 15
- 5. What is push pull amplifier? Write in detail about class B push amplifier? 15

SECTION - III

6. Write short note on :

15

- (a) Basic shunt regulator
- (b) IC voltage regulator

7. Explain twin tub CMOS process step by step along with neat diagram of each step? 15

SECTION – IV

8. (a) Draw and explain the block diagram of OP-AMP and characteristics of ideal OP-AMP. 10
- (b) What is common-mode configuration and CMRR? 5
9. (a) Write down a short note on astable operation of 555 timer. 8
- (b) What is DAC? Explain any *one* DAC in detail. 7
-