

Roll No.

3326

**B. Tech. 6th Semester (ECE)
Examination – May, 2023**

CMOS DESIGN

Paper : PCC-ECE-308-G

Time : Three Hours]

[Maximum Marks : 75

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Attempt *five* questions in all, selecting *one* question from each Unit. Question No. 1 is *compulsory*. All questions carry equal marks.

1. Explain the following : 2.5 × 6 = 15
- (a) Stick diagram
 - (b) Compare NMOS and PMOS transistor
 - (c) Sketch the transmission gate or pass gate
 - (d) MOSFET
 - (e) Latch
 - (f) CMOS

UNIT – I

2. (a) Illustrate ideal I-V characteristics of MOS transistors with necessary diagrams. 8
(b) Explain RC delay model. 7
3. Write short notes and draw stick diagram on the following :
- (a) CMOS Inverter 7
(b) NAND Gate 8

UNIT – II

4. (a) Compare the static CMOS inverter and Pseudo-nMOS inverters. 8
(b) Explain about the dynamic cascode voltage switch logic with neat diagram. 7
5. (a) Explain the following dynamic circuits. 8
(i) Domino logic
(ii) Dual-rail Domino logic
(b) Classify the various Static CMOS circuits for combinational circuits. 7

UNIT – III

6. (a) Discuss in detail about various pipelining techniques and explain in detail. 7
(b) Sketch the sense amplifiers based CMOS circuit. 8
7. (a) Write about Schmitt trigger and its properties. 8
(b) What is Astable sequential circuits. 7

UNIT – IV

8. Explain the following : 15
- (i) Shifters
 - (ii) ALUs
9. (a) Design a one transistor DRAM cell. 7
- (b) Draw and explain the architecture of large memory array. 8
-